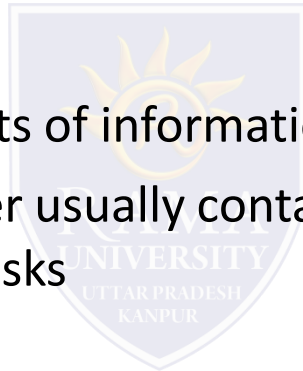




FACULTY OF ENGINEERING & TECHNOLOGY


Registers

- Registers like counters are clocked sequential circuits
- A register is a group of flip-flops
 - Each flip-flop capable of storing one bit of information
 - An n-bit register
 - consists of n flip-flops
 - capable of storing n bits of information
 - besides flip-flops, a register usually contains combinational logic to perform some simple tasks
 - In summary
 - flip-flops to hold information
 - combinational logic to control the state transition






Uses of Registers

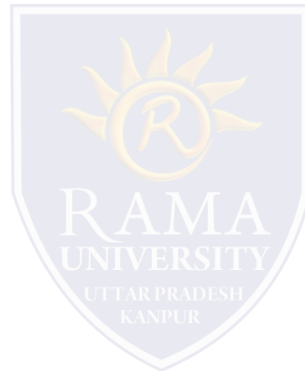- Registers are useful for storing and manipulating information
 - internal registers in microprocessors to manipulate data




4-bit Register

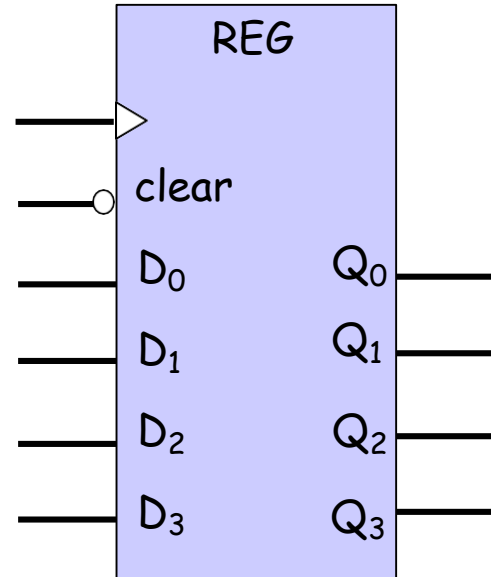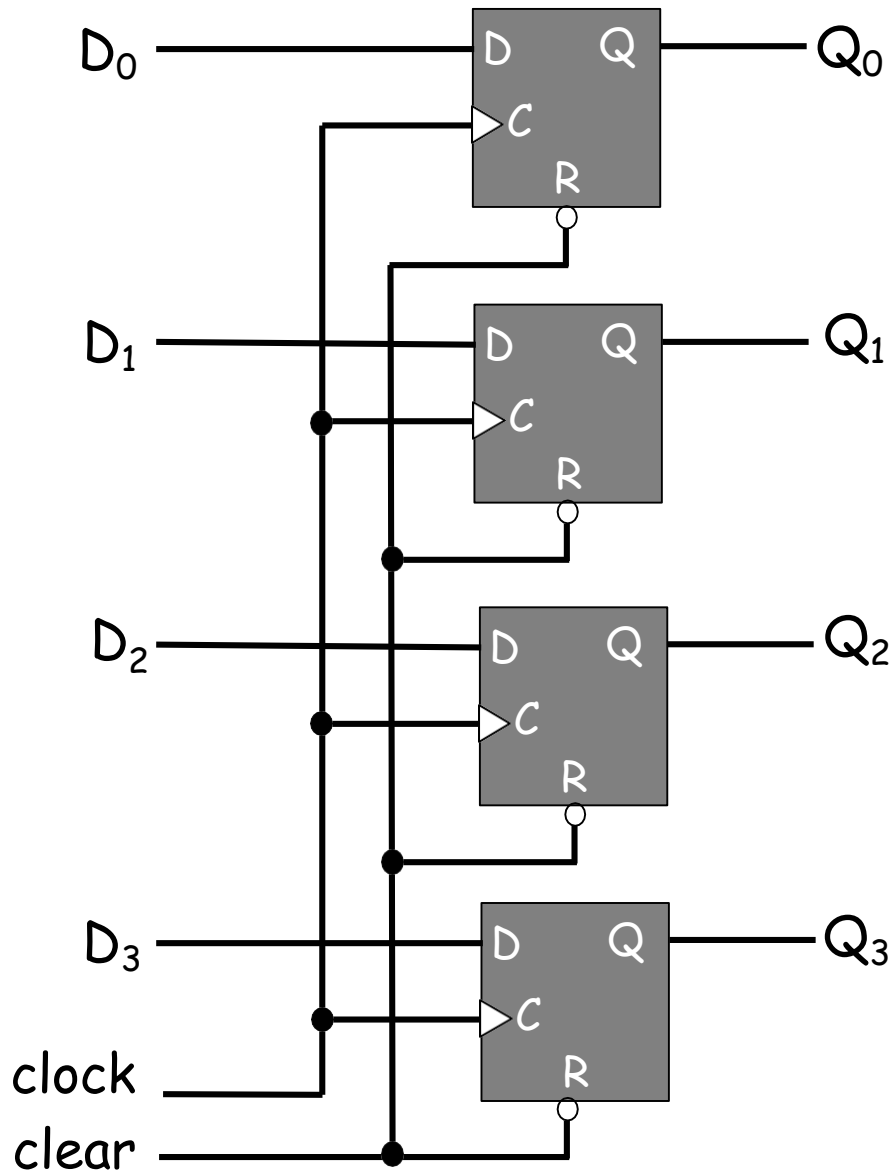


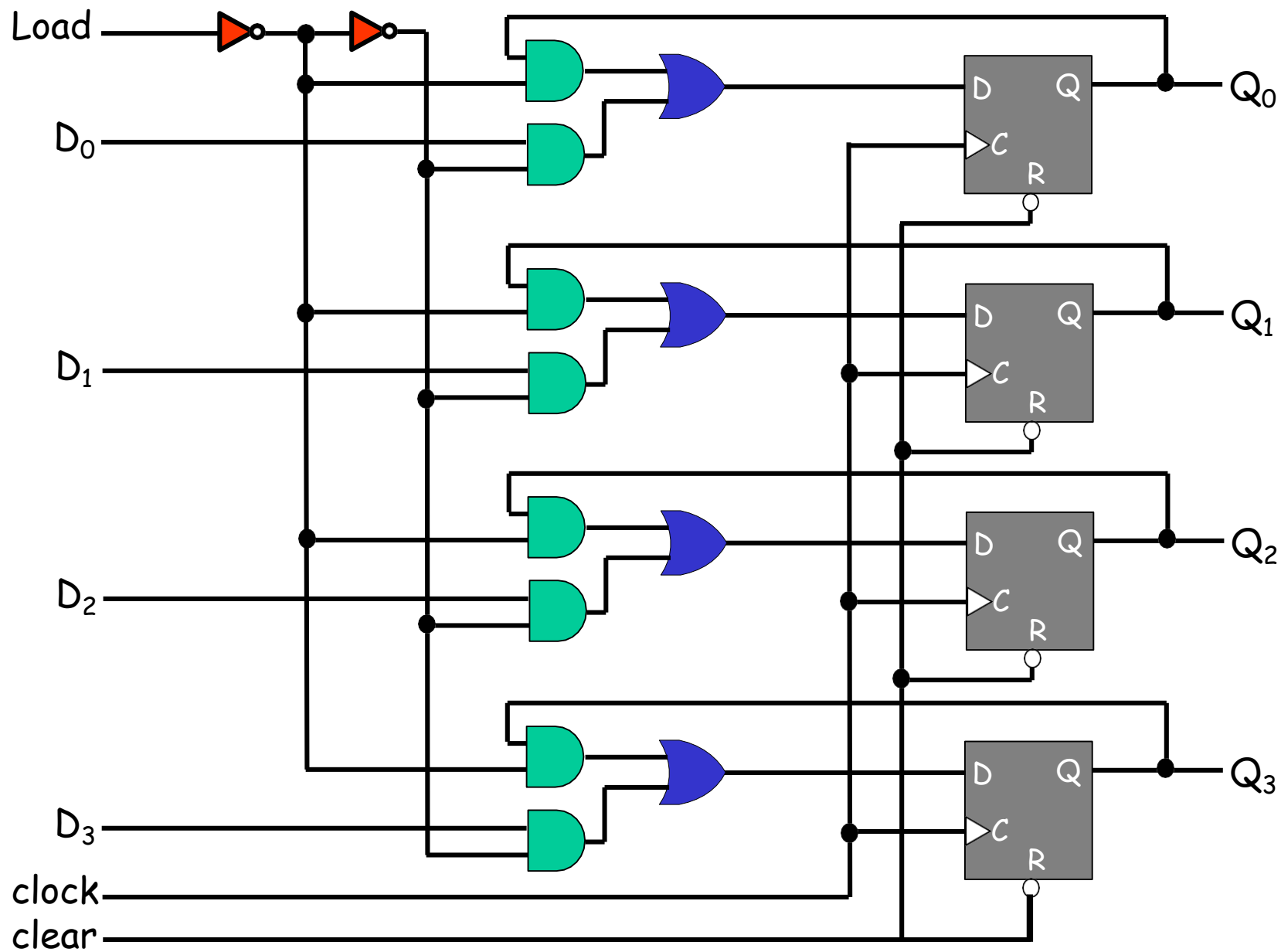


Loading Register

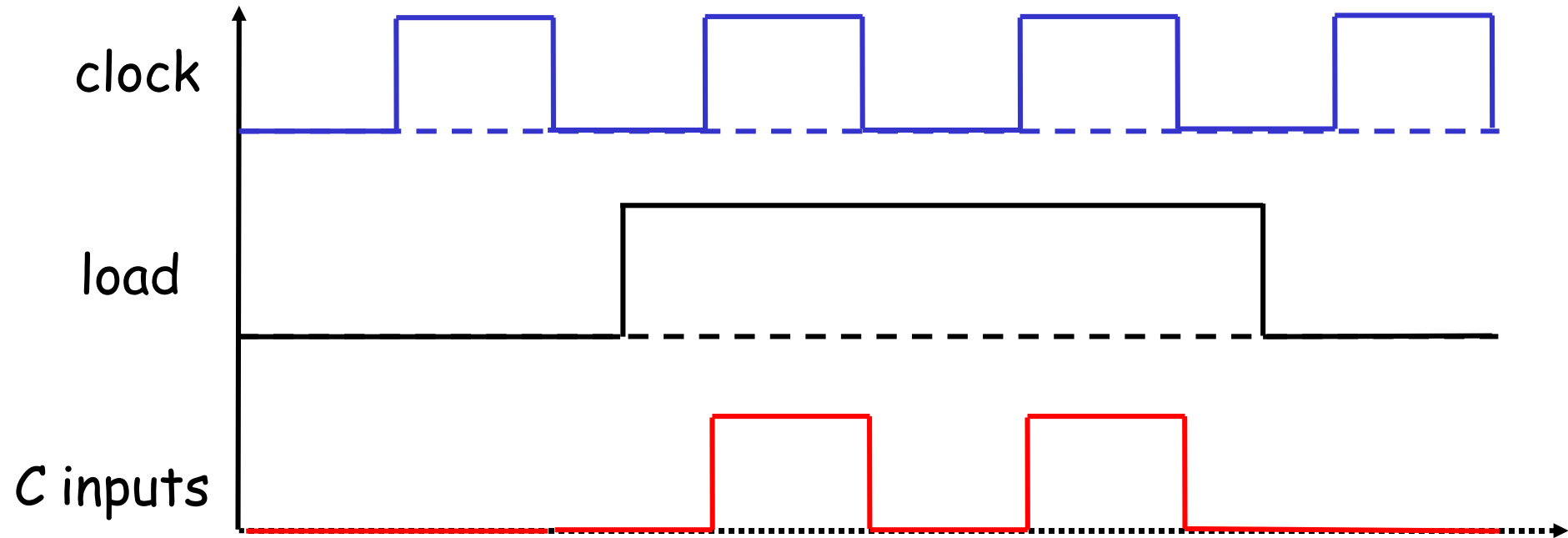

Register Transfer - 1

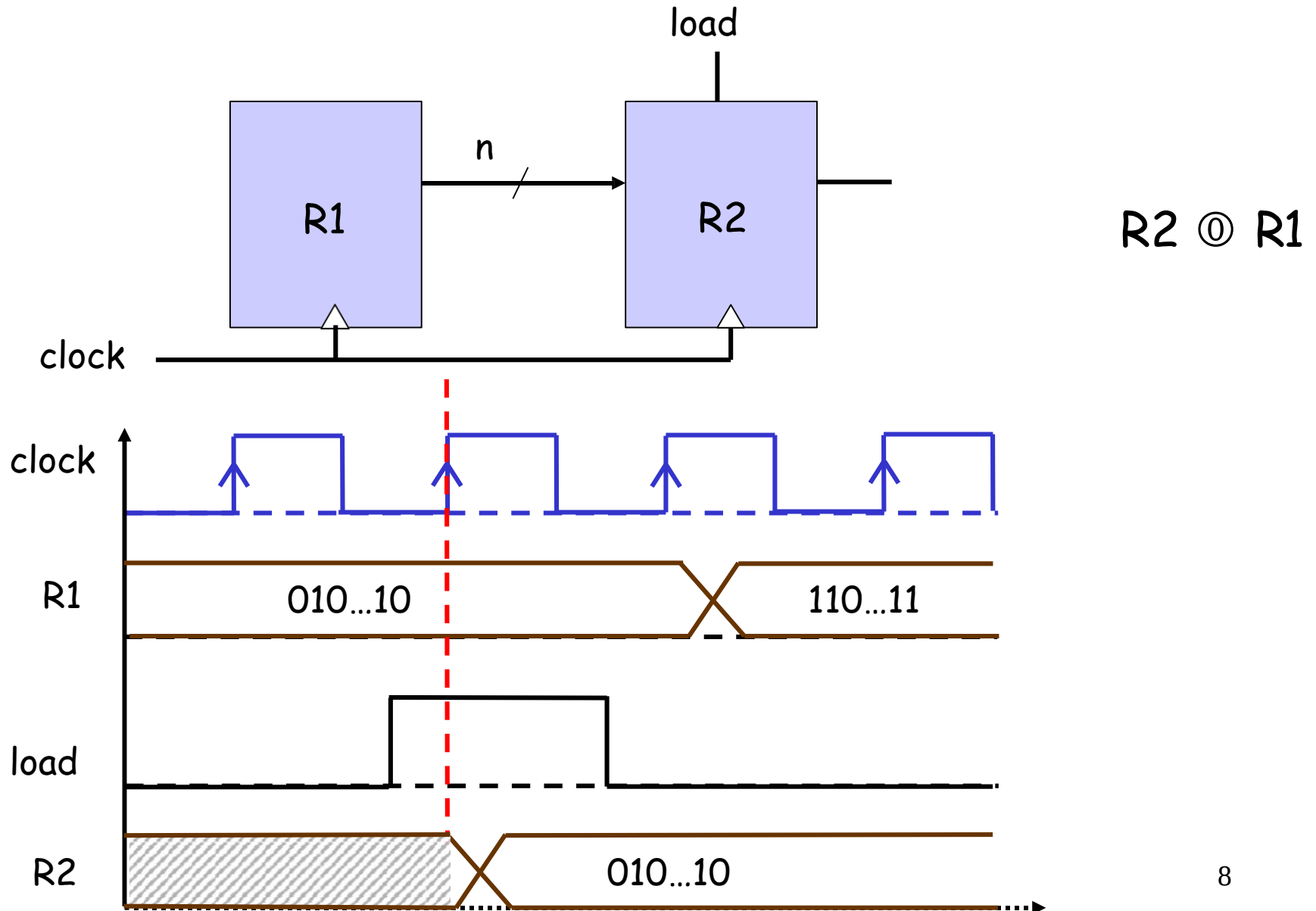


Register Transfer - 2

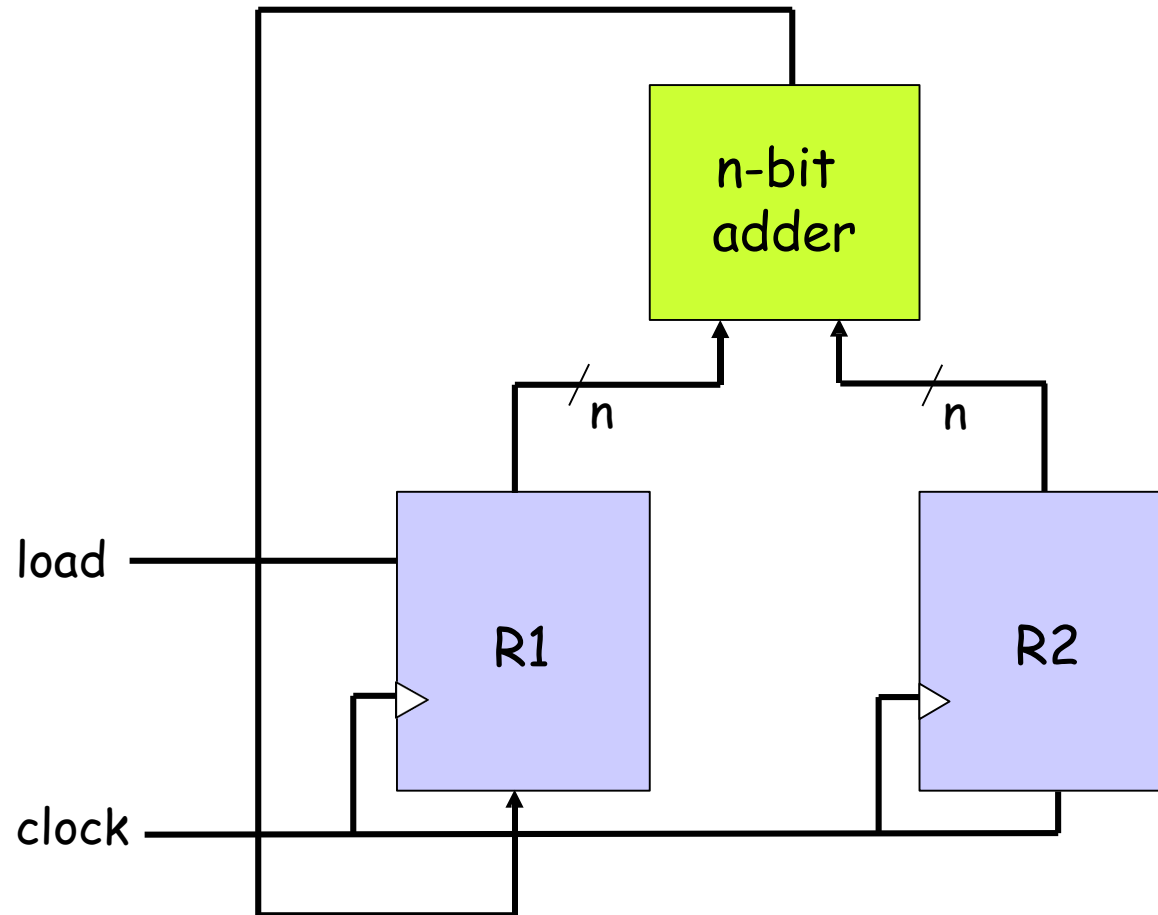


$R1 \leftarrow R1 + R2$

Datapath & Control Unit

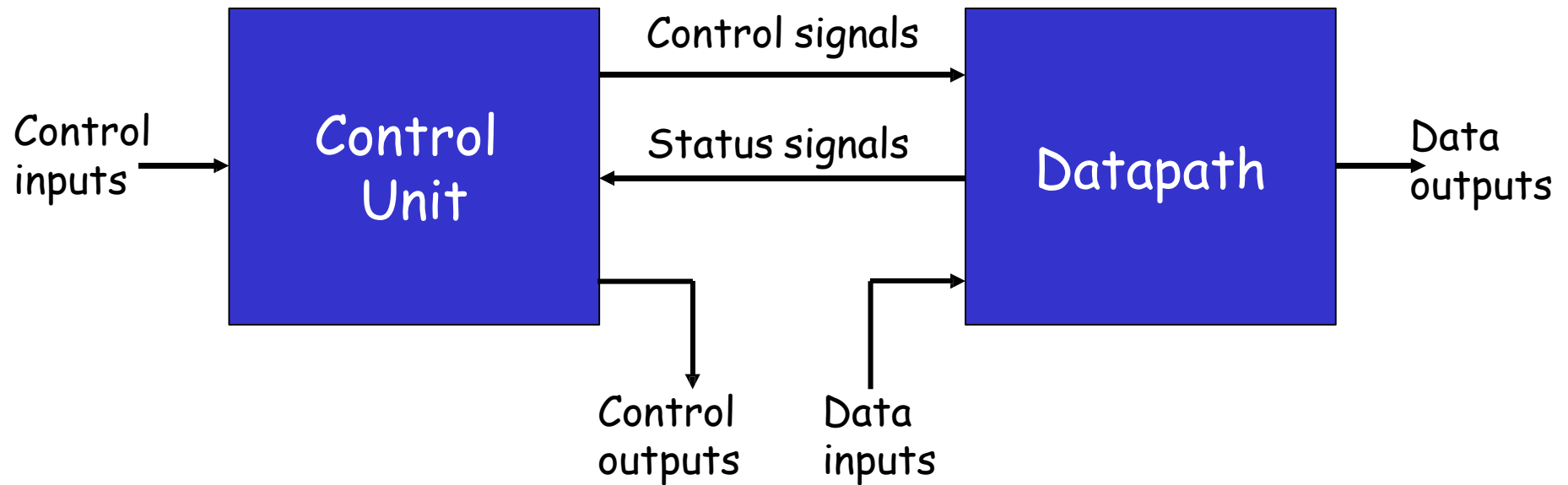

Shift Registers

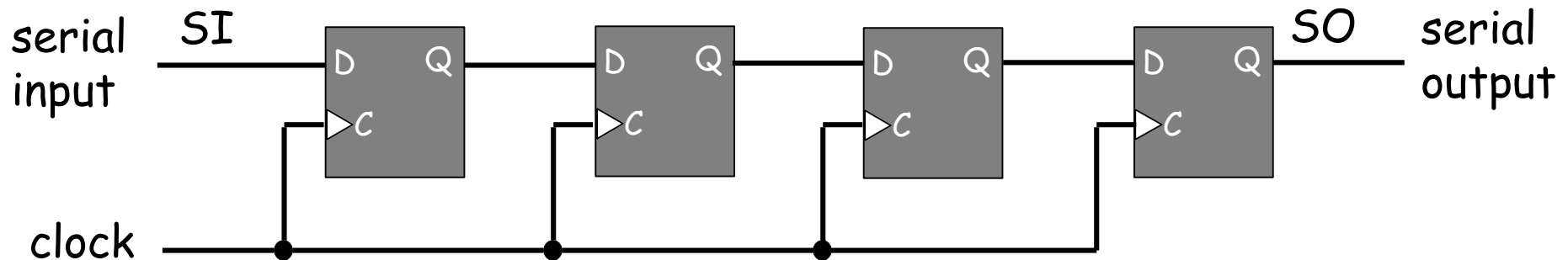
- A register capable of shifting its information in one or both directions
 - Flip-flops in cascade



- The current state can be output in n clock cycles

Serial Mode

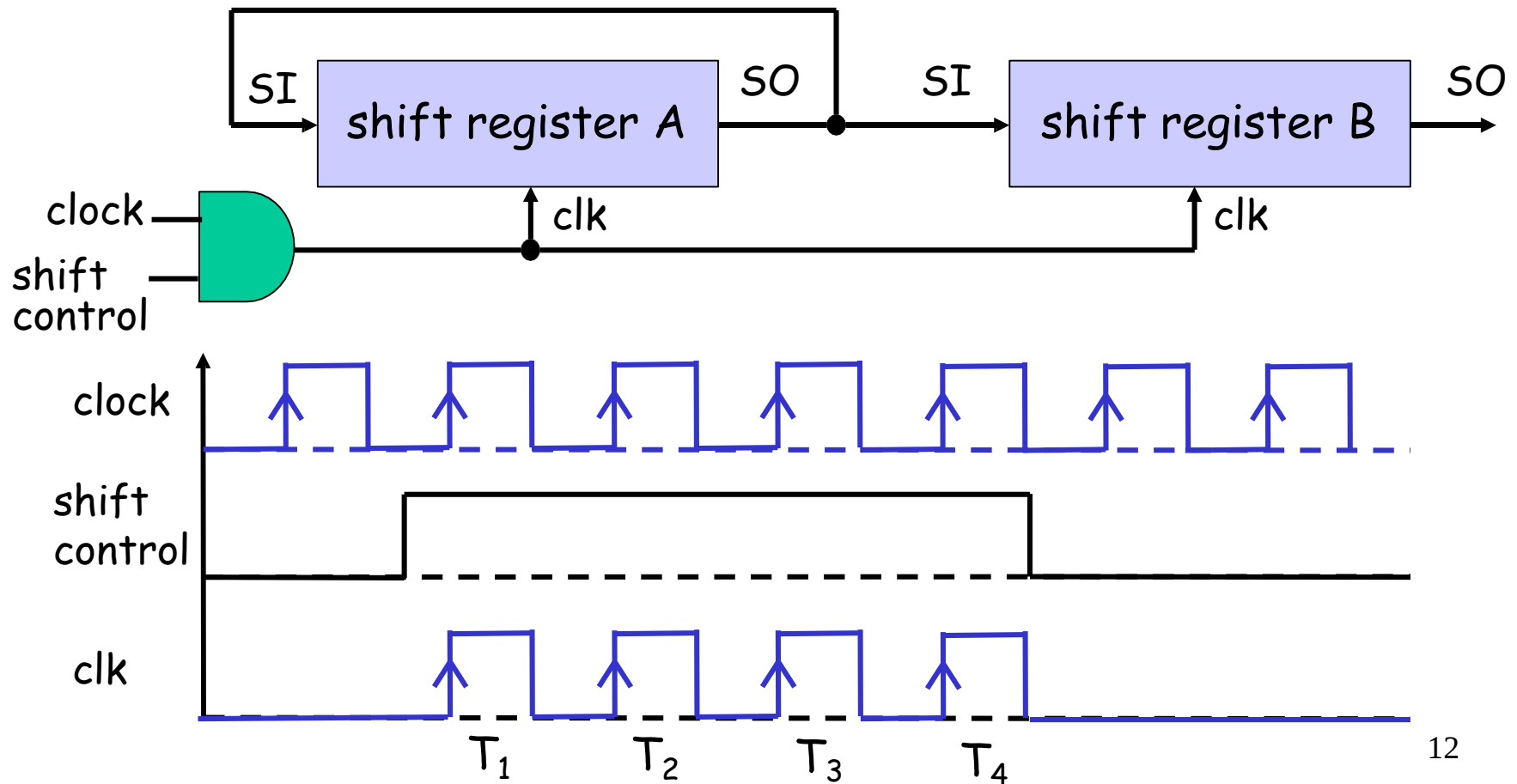- A digital system is said to operate in serial mode when information is transferred and manipulated one bit a time.



Serial Transfer


- Suppose we have two 4-bit shift registers

Timing pulse	Shift register A				Shift register B			
initial value	1	0	1	1	0	0	1	0
After T_1	1	1	0	1	1	0	0	1
After T_2	1	1	1	0	1	1	0	0
After T_3	0	1	1	1	0	1	1	0
After T_4	1	0	1	1	1	0	1	1

$B \odot A$


Serial Addition

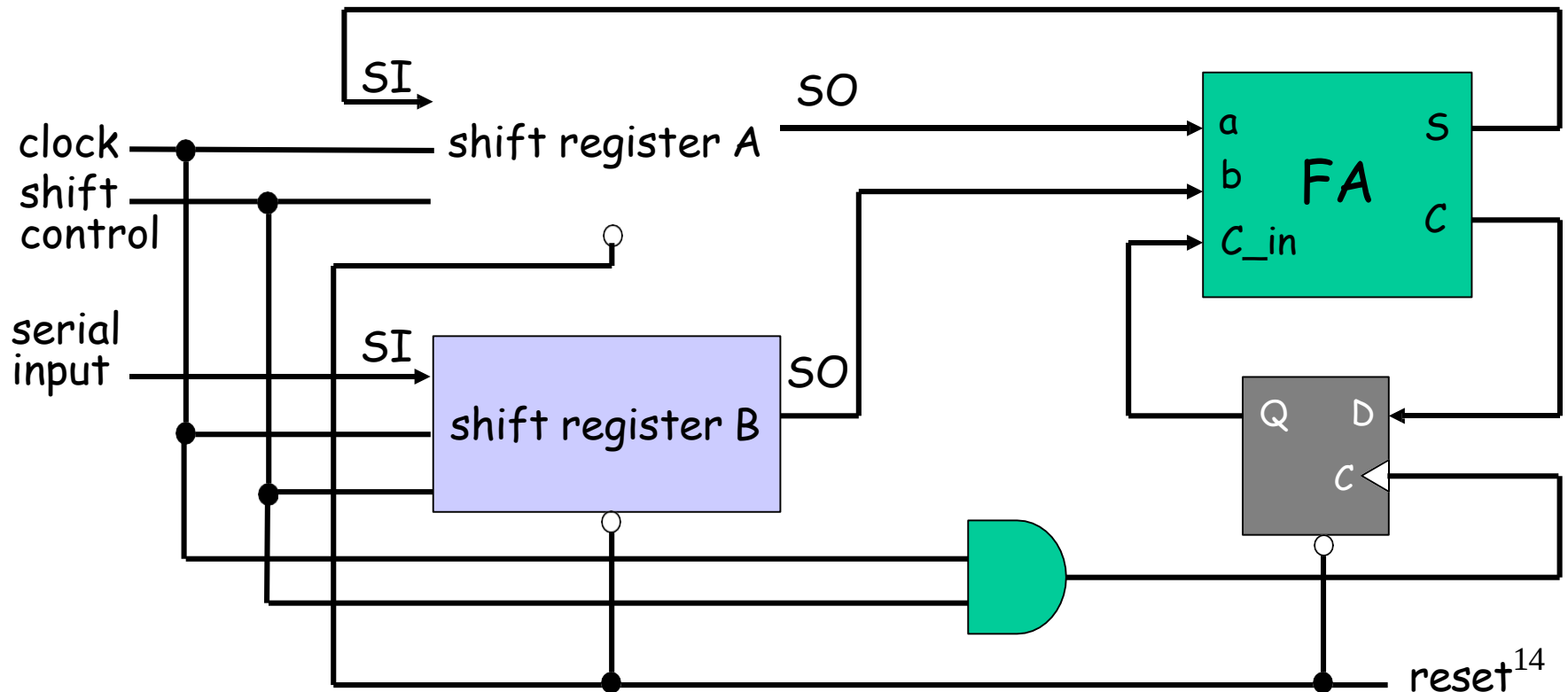- In digital computers, operations are usually executed in parallel, since it is faster
- Serial mode is sometimes preferred since it requires less equipment



Example: Serial Addition

- A and B are 2-bit shift registers

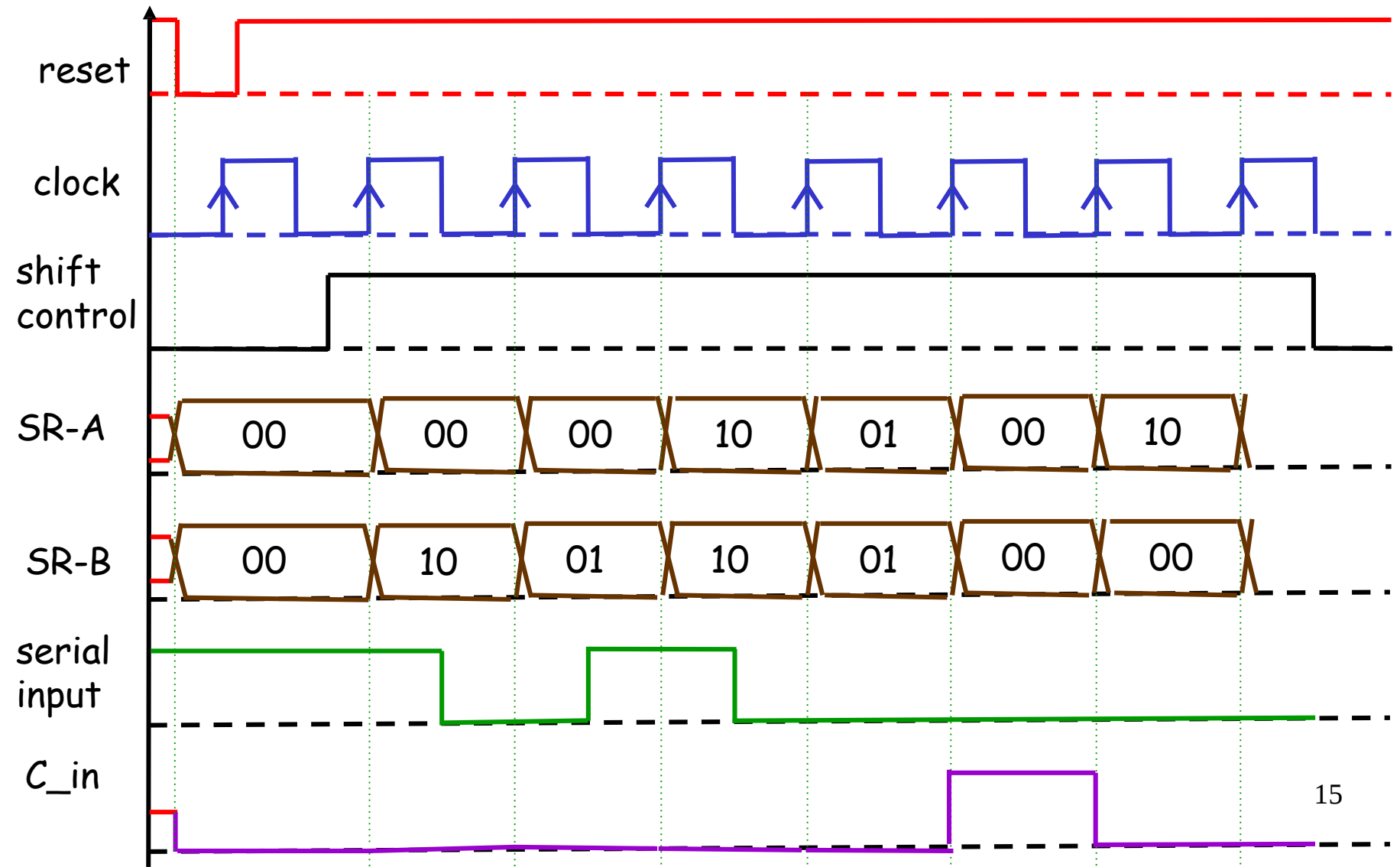

Designing Serial Adder - 1

$$Q(t+1) = JQ' + K'Q$$

Present state Q	Inputs x y		Next state Q	Output S	Flip-flop inputs J _Q K _Q	
0	0	0	0	0	0	X
0	0	1	0	1	0	X
0	1	0	0	1	0	X
0	1	1	1	0	1	X
1	0	0	0	1	X	1
1	0	1	1	0	X	0
1	1	0	1	0	X	0
1	1	1	1	1	X	0

$$J_Q = xy$$

$$K_Q = x'y' = (x + y)'$$


$$S = x \oplus y \oplus Q$$

Designing Serial Adder - 2

$$J_Q = xy$$

$$K_Q = x'y' = (x + y)'$$

$$S = x \oplus y \oplus Q$$

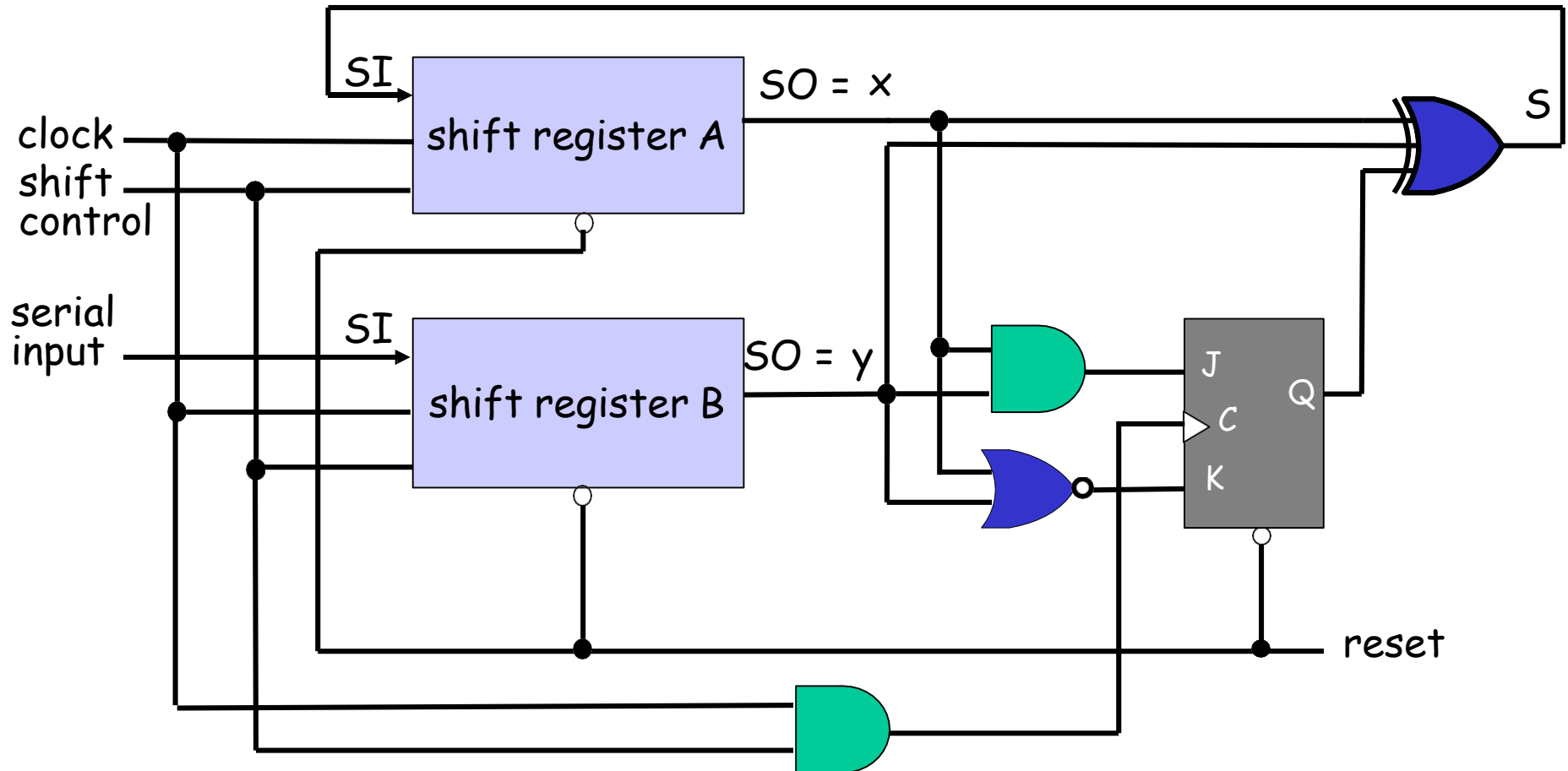

Universal Shift Register

- Capabilities:
 1. *A clear control to set the register to 0.*
 2. *A clock input*
 3. *A shift-right control*
 4. *A shift-left control*
 5. *n input lines*
 6. *A parallel-load control*
 7. *n parallel output lines*
 8. *A shift-control*

Universal Shift Register

parallel outputs

