



FACULTY OF ENGINEERING & TECHNOLOGY

LOGIC GATE

Logic gates are used to carry out logical operations on single or multiple binary inputs & give one binary output. In simple terms, logic gates are the electronic circuits in a digital system.

Truth Table

A truth table shows how a logic circuit's output responds to various combinations of the inputs, using logic 1 for true and logic 0 for false.

Type of Logic Gate


There are three types of logic gate

1. Basic Gate (AND, OR & NOT)
2. Universal Gate (NAND & NOR)
3. Arithmetic Gate (EXOR & EXNOR)

1. Basic Gate

• AND Gate:


In AND gate the output of an AND gate attains the state 1 if and only if all the inputs are in state 1.

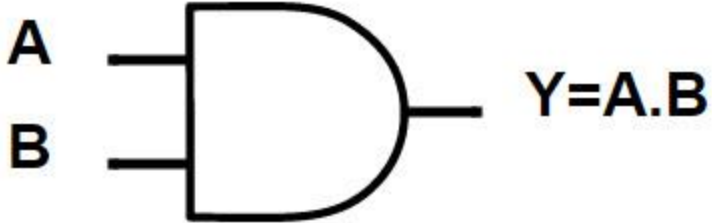Symbol	Truth Table															
<p>2-input AND Gate</p>  <p>A</p> <p>B</p> <p>Y = A.B</p>	<table border="1"><thead><tr><th>A</th><th>B</th><th>Y</th></tr></thead><tbody><tr><td>0</td><td>0</td><td>0</td></tr><tr><td>0</td><td>1</td><td>0</td></tr><tr><td>1</td><td>0</td><td>0</td></tr><tr><td>1</td><td>1</td><td>1</td></tr></tbody></table>	A	B	Y	0	0	0	0	1	0	1	0	0	1	1	1
	A	B	Y													
	0	0	0													
	0	1	0													
	1	0	0													
1	1	1														
Boolean Expression Y = A.B	Read as A AND B gives Y															

NUMBER SYSTEM


- **OR Gate:**

In OR gate the output of an OR gate attains the state 1 if one or more inputs attain the state 1.

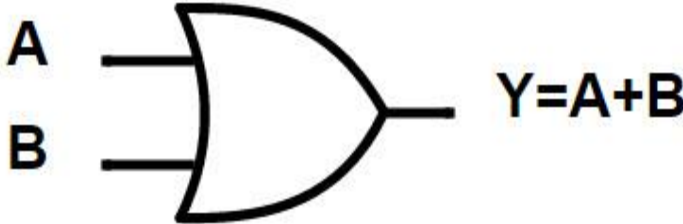Symbol	Truth Table		
<p>2-input OR Gate</p>  <p>$Y = A + B$</p>	A	B	Y
	0	0	0
	0	1	1
	1	0	1
	1	1	1
Boolean Expression $Y = A + B$	Read as A OR B gives Y		

- **NOT Gate:**

In NOT gate the output of a NOT gate attains the state 1 if and only if the input does not attain the state 1.

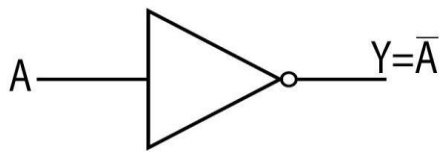
Symbol	Truth Table	
 <p>$Y = \bar{A}$</p>	A	Y
	0	1
	1	0
Boolean Expression $Y = \text{not } A$ or \bar{A}	Read as inverse of A gives Y	

NUMBER SYSTEM

2. Universal Gate:

- **NAND Gate**


This gate is the combination of AND & NOT gate.

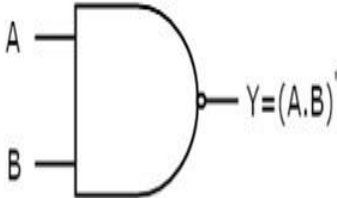Symbol	Truth Table		
2-input NAND Gate	A	B	Y
	0	0	1
	0	1	1
	1	0	1
	1	1	0
	Boolean Expression $Y = (A \cdot B)'$	Read as A NAND B gives Y	

NUMBER SYSTEM

•NOR Gate

This gate is the combination of OR & NOT gate.

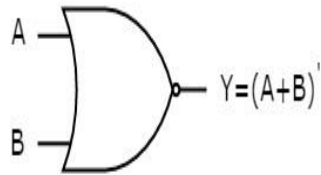Symbol	Truth Table		
2-input NAND Gate 	A	B	Y
	0	0	1
	0	1	0
	1	0	0
	1	1	0
Boolean Expression $Y = (A + B)'$	Read as A NOR B gives Y		