



## FACULTY OF ENGINEERING & TECHNOLOGY

**Dileep Kumar**


Assistant Prof. EE Deptt

# A/D & D/A CONVERTERS

## Digital to Analog Conversion (DAC)
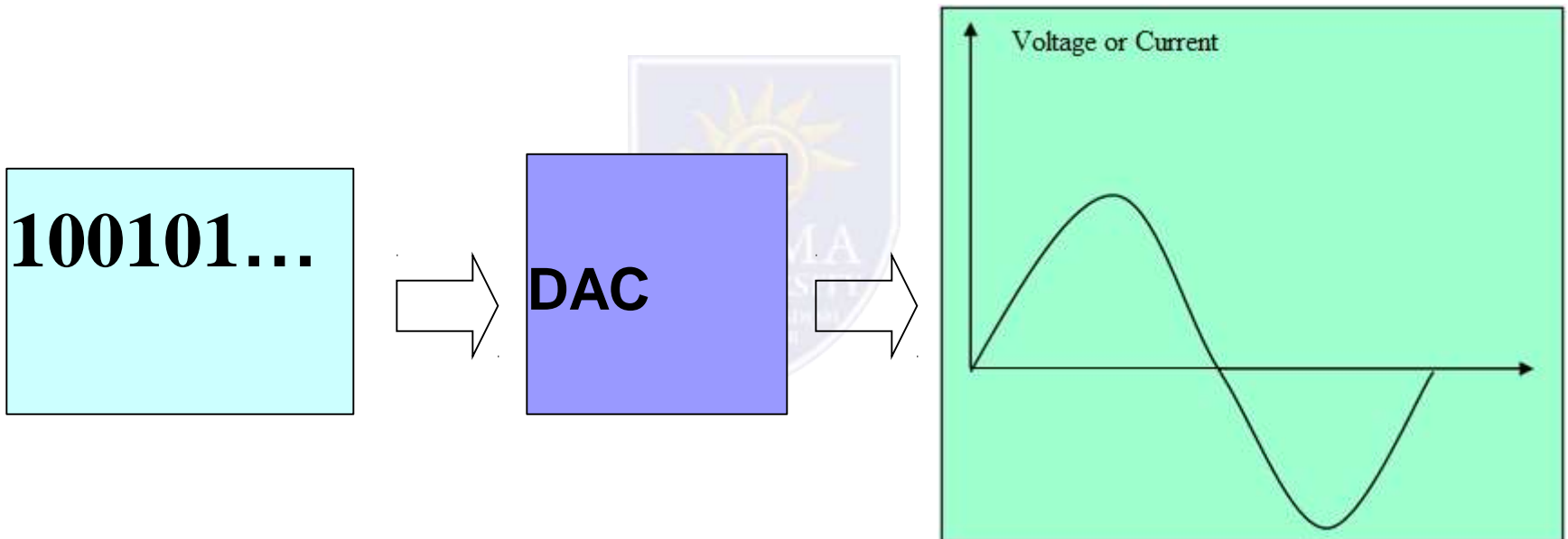
### What is a DAC?

A digital-to-analog converter (DAC) takes a digital code( generally binary number) as its input and produces an analog voltage or current as its output. This analog output is proportional to the digital input.



The input may be of n-bit long having different voltage levels. So in the D/A converters some method is to be used which can convert this voltage level of n-bits to its equivalent analog form.

Following two types of resistive networks are basically used for this purpose:

- i. Resistive Divider Network or weighted resistor network
- ii. Binary Ladder Network or R-2R network

The converter which comprises the resistive divider network is known as Resistive divider D/A converter and the D/A converter which comprises the binary ladder network is known as binary ladder D/A converter.




# A/D & D/A CONVERTERS

Converting discrete signals into discrete analog values that represent the magnitude of the input signal compared to a standard or reference voltage

- The output of the DAC is discrete analog steps.
- By increasing the resolution (number of bits), the step size is reduced, and the output approximates a continuous analog signal.

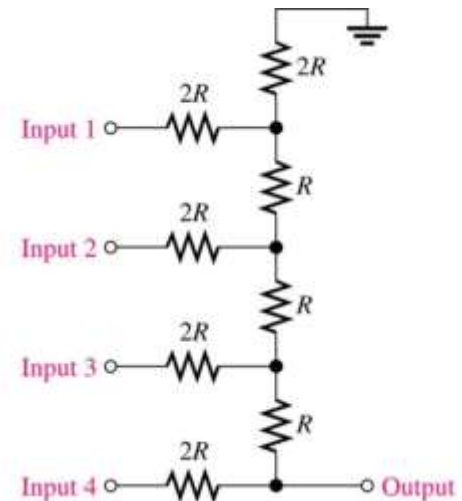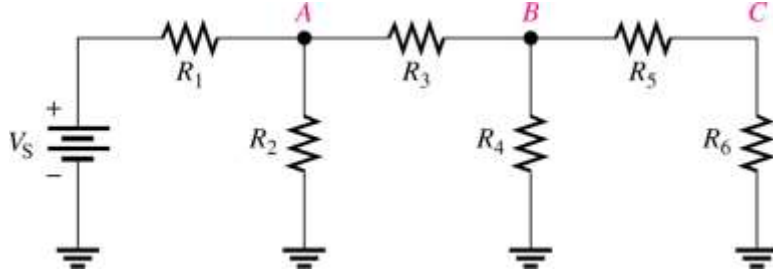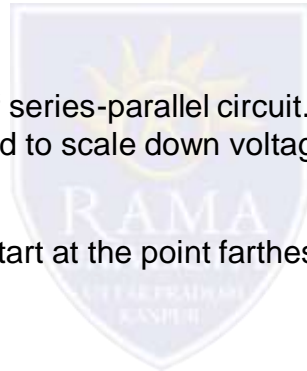
## Analysis of a Ladder Network

- A resistive ladder network is a special type of series-parallel circuit.
- One form of ladder network is commonly used to scale down voltages to certain weighted values for digital-to-analog conversion  
    Called R/2R Ladder Network
- To find total resistance of a ladder network, start at the point farthest from the source and reduce the resistance in steps.




# A/D & D/A CONVERTERS


## The R/R2 Ladder Network

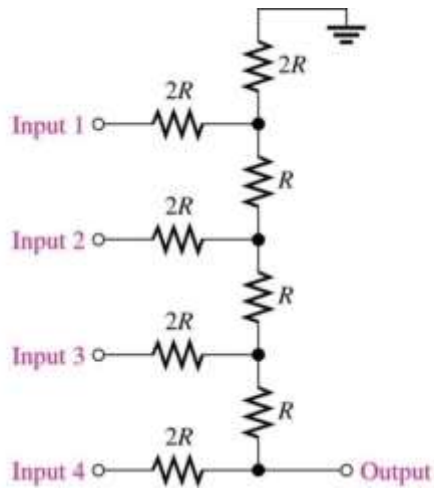

Only Input 4 is HIGH

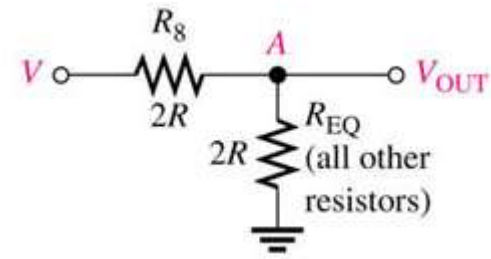

Only Input 3 is HIGH

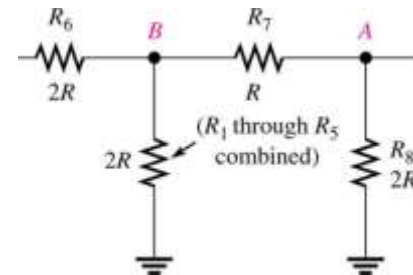

Used for Digital-to-analog converter

