




FACULTY OF ENGINEERING & TECHNOLOGY

Dileep Kumar

Assistant Prof. EE Deptt

A/D & D/A CONVERTERS

Example

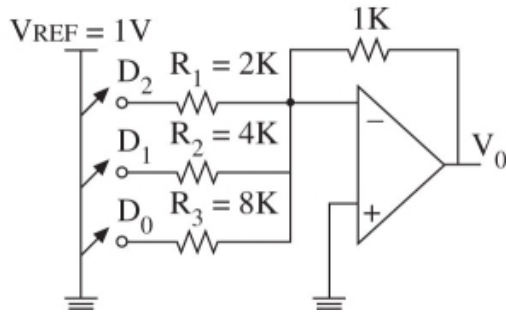

- If the reference voltage is 1 V, and if all switches are connected, the output current can be calculated as follows:
- Output voltage

$$I_o = I_T = I_1 + I_2 + I_3 = \frac{V_{REF}}{R_1} + \frac{V_{REF}}{R_2} + \frac{V_{REF}}{R_3} = \frac{V_{REF}}{1k} \left(\frac{1}{2} + \frac{1}{4} + \frac{1}{8} \right) = 0.875mA$$

$$V_o = -R_f I_T = -(1k) \times (0.875mA) = -0.875V = \left| \frac{7}{8} V \right|$$

A/D & D/A CONVERTERS

D/A Converters as Integrated Circuits

- D/A converters are available commercially as integrated circuits
- Can be classified in three categories.
 - Current output, voltage output, and multiplying type
 - Current output DAC provides the current I_o as output signal
 - Voltage output D/A converts I_o into voltage internally by using an op amp and provides the voltage as output signal
 - In multiplying DAC, the output is product of the input voltage and the reference source V_{REF} .
 - Conceptually, all three types are similar

