



RAMA  
UNIVERSITY

[www.ramauniversity.ac.in](http://www.ramauniversity.ac.in)

FACULTY OF ENGINEERING & TECHNOLOGY

Electrical Machine-1

Amit Kumar Singh

# SINGLE PHASE TRANSFORMER


## Principle of Operation

The primary of the transformer having  $N_1$  turns is fed from an AC supply of  $V_1$  volts. The current  $I_1$  will flow through the primary coil. The current through the primary will set up a flux  $\phi$  in the core. This flux, when linked with the primary winding, will produce an induced e.m.f.,  $E_1$ , in the primary.

The flux  $\phi$  will pass through the core and link with the secondary winding to induce an e.m.f.,  $E_2$ , in the secondary winding. Because of this induced e.m.f., a current  $I_2$  will flow through the load connected with the secondary winding. The load terminal voltage is  $V_2$ .

If the input voltage  $V_1$  is greater than the output voltage  $V_2$ , then it is called the step-down transformer. If the input voltage  $V_1$  is less than the output voltage  $V_2$ , then it is called the step-up transformer.

## EMF equation

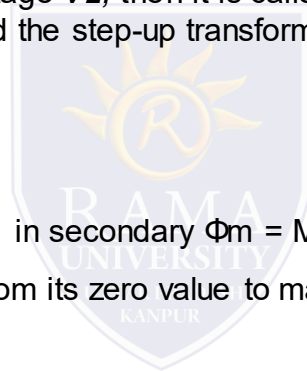

Let  $N_1$  = No. of turns in primary  $N_2$  = No. of turns in secondary  $\Phi_m$  = Maximum flux in core in webers =  $B_m \times A$

$f$  = Frequency of a.c. input in Hz flux increases from its zero value to maximum value  $\Phi_m$  in one quarter of the cycle i.e. in  $1/4 f$  second.

$\therefore$  Average rate of change of flux =  $1/4 f \Phi_m = 4 f \Phi_m$  Wb/s or volt Now, rate of change of flux per turn means induced e.m.f. in volts.

$\therefore$  Average e.m.f./turn =  $4 f \Phi_m$  volt If flux  $\Phi$  varies sinusoidally, then r.m.s. value of induced e.m.f. is obtained by multiplying the average value with form factor. Form factor = r.m.s. value/ avg. value = 1.11

$\therefore$  r.m.s. value of e.m.f./turn =  $1.11 \times 4 f \Phi_m = 4.44 f \Phi_m$  volt • Now, r.m.s. value of the induced e.m.f. in the whole of primary winding = (induced e.m.f./turn)  $\times$  No. of primary turns


$$\bullet E_1 = 4.44 f N_1 \Phi_m = 4.44 f N_1 B_m A \dots \dots (1)$$

Similarly, r.m.s. value of the e.m.f. induced in secondary is,


$$\bullet E_2 = 4.44 f N_2 \Phi_m = 4.44 f N_2 B_m A \dots \dots (2)$$

# SINGLE PHASE TRANSFORMER

## Practical Transformer on No Load

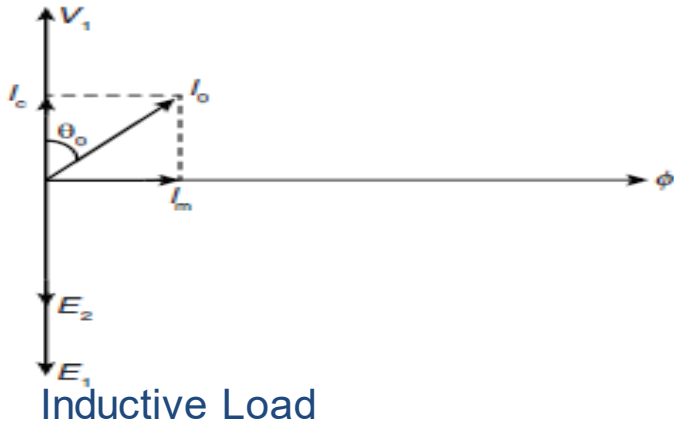

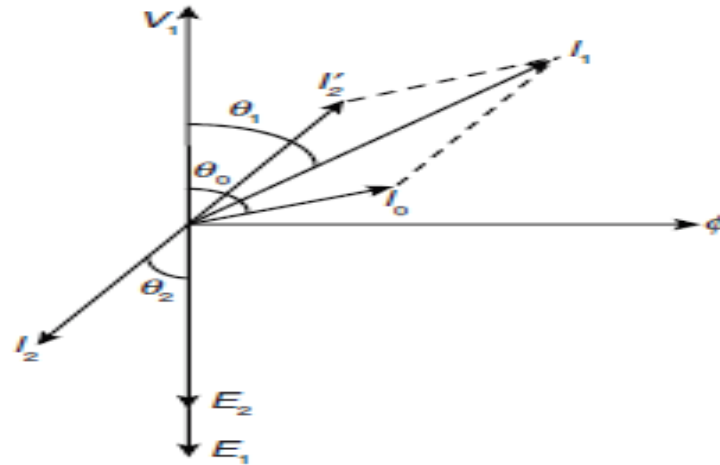- i) The magnetisation component ( $I_m$ ), which is responsible for the production of flux in the core.
- ii) The power component ( $I_w$ ), which will supply the total losses.



# SINGLE PHASE TRANSFORMER

## Phasor Diagram of Transformer on Load

Capacitive Load

