



FACULTY OF ENGINEERING & TECHNOLOGY




Dileep Kumar

Assistant Prof. EE Deptt


A/D & D/A CONVERTERS

Analog to Digital (A/D) Converter

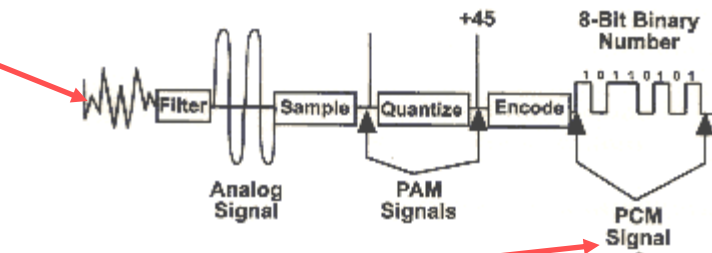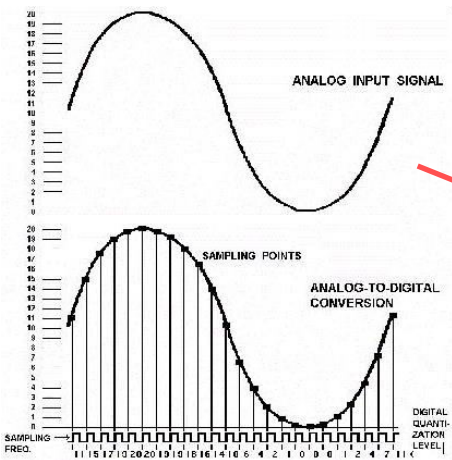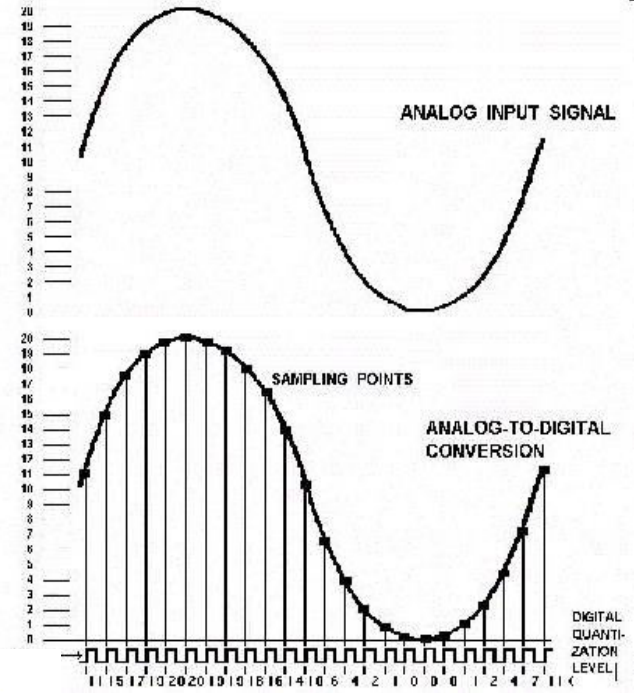- In order to change an analog signal to digital, the input analog signal is sampled at a high rate of speed.
- The amplitude at each of those sampled moments is converted into a number equivalent – this is called quantization.
- These numbers are simply the combinations of the 0s and 1s used in computer language – this called encoding.



Modulation

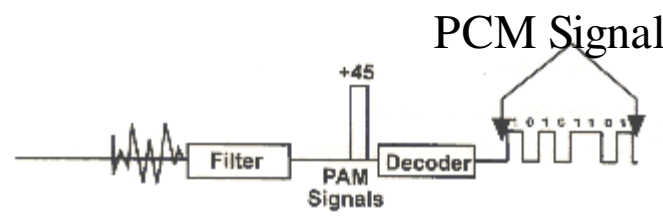


Demodulation

A/D & D/A CONVERTERS

Analog-to-Digital

- A simple hypothetical A/D converter circuit with one analog input signal and three digital output lines with eight possible binary combinations: 000 to 111
 - Shows the graph of digital output for FS V analog input
- The following points can be summarized in the above process:
 - Maximum value this quantization process reaches is $7/8$ V for a 1 V analog signal; includes $1/8$ V an inherent error
 - $1/8$ V (an inherent error) is also equal to the value of the Least Significant Bit (LSB) = 001.
 - Resolution of a converter is defined in terms of the number of discrete values it can produce; also expressed in the number of bits used for conversion or as $1/2^n$ where n = number of bits
 - The value of the most significant bit (MSB) -100- is equal to $1/2$ the voltage of the full-scale value of 1 V.
 - The value of the largest digital number 111 is equal to full-scale value minus the value of the LSB.
 - The quantization error can be reduced or the resolution can be improved by increasing the number of bits used for the conversion

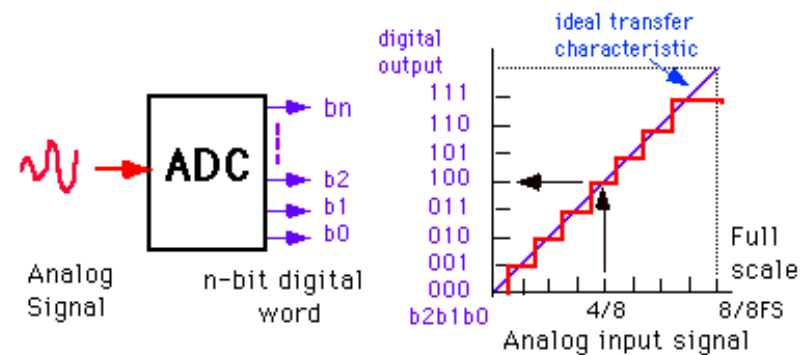

A/D & D/A CONVERTERS

A/D Conversion - Types

Can be classified in four groups:

1. Integrator:

- Charges a capacitor for a given amount of time using the analog signal.
- It discharges back to zero with a known voltage and the counter provides the value of the unknown signal.
- Provides slow conversion but low noise.
- Often used in monitoring devices (e.g., voltmeters)

2. Flash: uses multiple comparators in parallel.

- The known signal is connected to one side of the comparator and the analog signal to be converted to the other side of the comparator.
- The output of the comparators provides the digital value.
- This is a high-speed, high cost converter.

3. Successive approximation:

Includes a D/A (digital to analog) converter and a comparator. An internal analog signal is generated by turning on successive bits in the D/A converter.

4. Counter:

Similar to a successive approximation converter except that the internal analog signal is generated by a counter starting at zero and feeding it to the D/A converter.