




## FACULTY OF ENGINEERING & TECHNOLOGY

Dileep Kumar  
Assistant Prof. EE Deptt

# COMBINATIONAL CIRCUITS
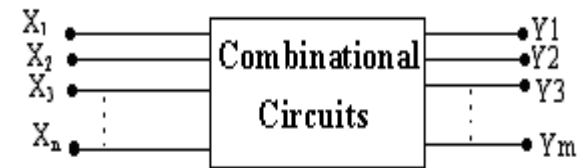
## Combinational Circuits

The combinational circuits are the network of logic gates having a set of input independent variables, and outputs as the Boolean functions inputs. The output variables in these circuits depend only on the present value of the inputs and do not depend upon their previous values.



## Half Adder

A half adder is combinational circuits which adds two binary digits simultaneously

### Circuit Diagram Truth Table


Inputs		Outputs	
A	B	S	C
0	0	0	0
0	1	1	0
1	0	1	0
1	1	1	1

Sum S and Carry C are given by

$$S = \bar{A} \cdot B + A \cdot \bar{B}$$

$$= A \oplus B$$

$$C = A \cdot B$$

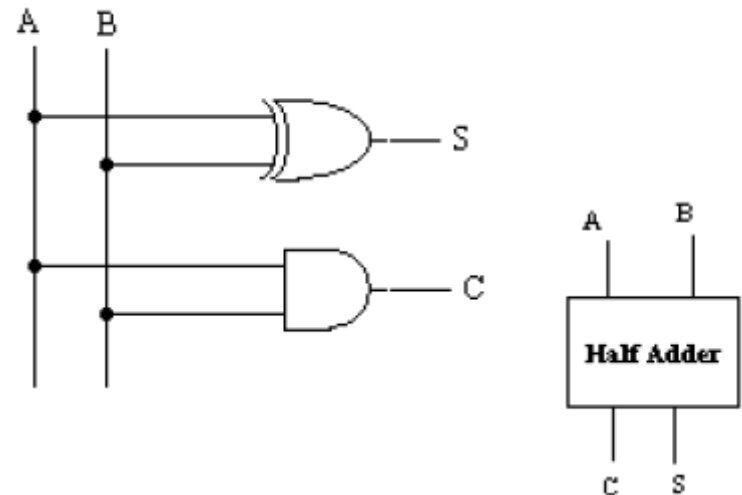

Symbolic representation of the half adder

Q1: Design the half adder using NOR gates only.

# COMBINATIONAL CIRCUITS


## Full Adder

A Full adder is combinational circuits which adds three binary digits simultaneously

### Circuit Diagram

### Truth Table

A <sub>1</sub>	B <sub>1</sub>	C <sub>0</sub>	S <sub>1</sub>	C <sub>1</sub>
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

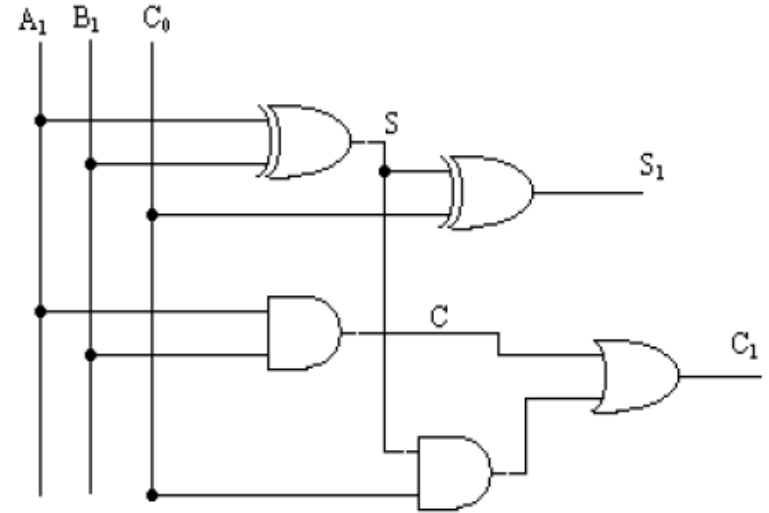

Sum S1 & Carry C<sub>1</sub> are given by

$$S_1 = A_1 \oplus B_1 \oplus C_0$$

$$C_1 = (A_1 \oplus B_1)C_0 + A_1B_1$$

It is clear that a full adder consists of two half adders and an OR gate

