



FACULTY OF ENGINEERING & TECHNOLOGY

Dileep Kumar
Assistant Prof. EE Deptt

COUNTER



Counter

- Counters, consisting of a number of flip-flops, count a stream of pulses applied to the counter's CK input.
- The output is a binary value whose value is equal to the number of pulses received at the CK input.
- The size of the output word depends on the number of flip-flops that make up the counter.
- The output lines of a 4-bit counter represent the values 2⁰, 2¹, 2² and 2³, or 1, 2, 4 and 8 respectively.
- There are type of counter

1. Asynchronous Counter
2. Synchronous Counter

1. Asynchronous Counter


4-Bit Asynchronous Up Counter

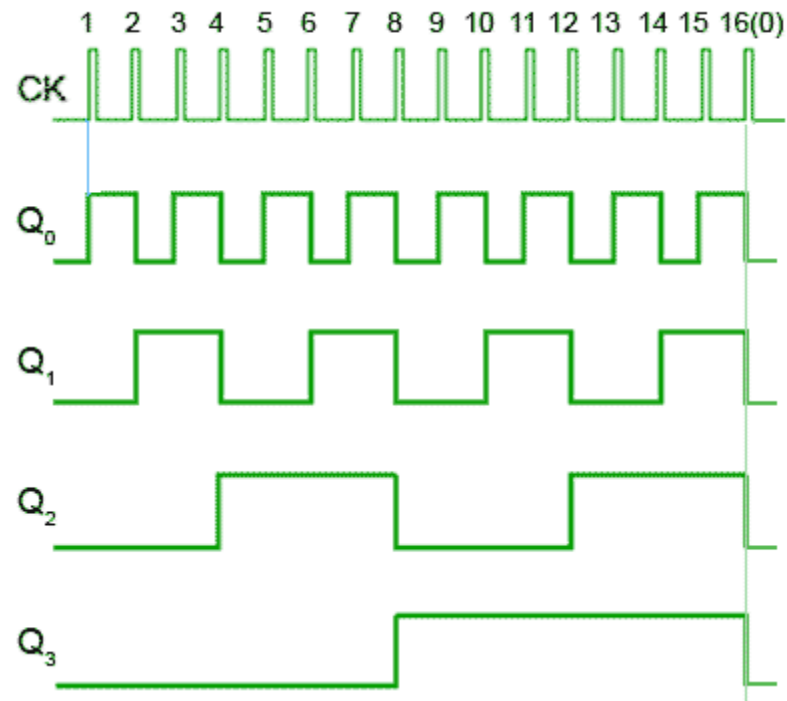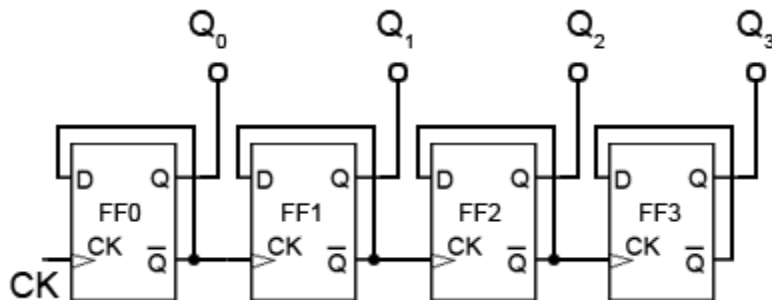

4-bit Asynchronous Up Counter Waveforms

COUNTER

Four Bit Asynchronous Down Counter

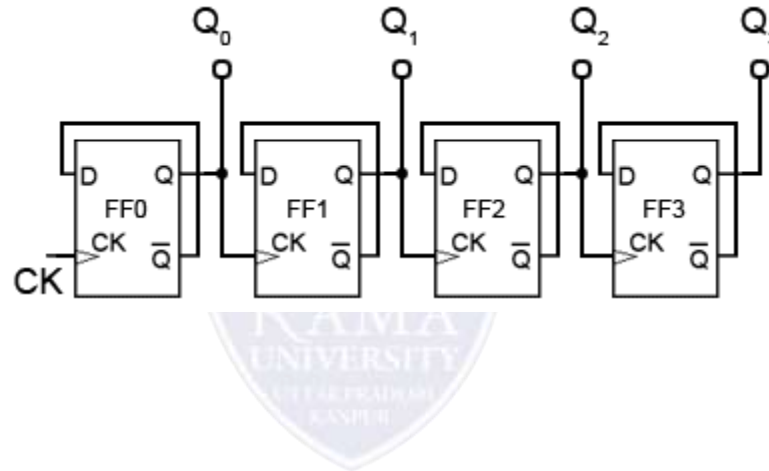

Synchronous Counters

The synchronous counter provides a more reliable circuit for counting purposes, and for high-speed operation, as the clock pulses in this circuit are fed to every flip-flop in the chain at exactly the same time. Synchronous counters use JK flip-flops, as the programmable J and K inputs allow the toggling of individual flip-flops to be enabled or disabled at various stages of the count. Synchronous counters therefore eliminate the clock ripple problem, as the operation of the circuit is synchronised to the CK pulses, rather than flip-flop outputs.

COUNTER

Synchronous Up Counter


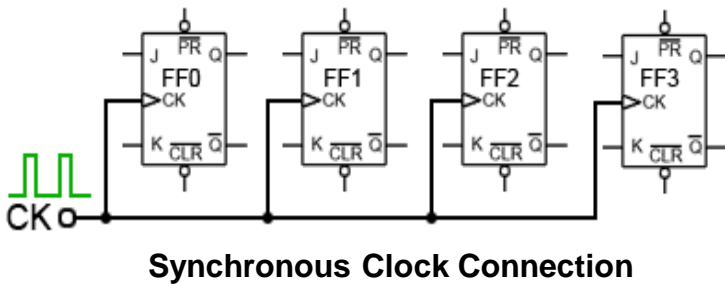
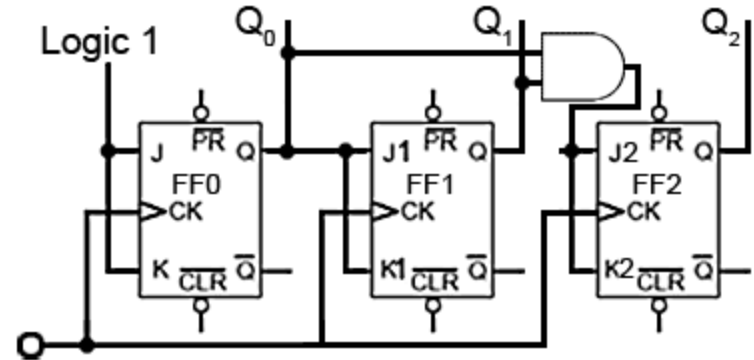


Table 5.6.1					
CK	Q ₀	Q ₁	J1	K1	After the CK pulse
0	0	0	0	0	No CK pulses yet
1	1	0	1	1	Q ₀ toggles making J1 & K1 = 1
2	0	1	0	0	Q ₀ & Q ₁ toggle making J1 & K1 = 0
3	1	1	1	1	Only Q ₀ toggles making J1 & K1 = 1
4	0	0	0	0	Q ₀ & Q ₁ toggle making J1 & K1 = 0

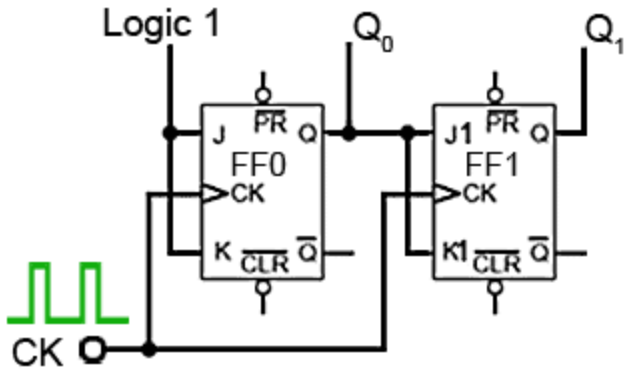

The First Two Stages of a Synchronous Counter

Adding a Third Stage