



RAMA  
UNIVERSITY

[www.ramauniversity.ac.in](http://www.ramauniversity.ac.in)

FACULTY OF ENGINEERING & TECHNOLOGY

Electrical Machine-1

Amit Kumar Singh

# SINGLE PHASE TRANSFORMER

## Transformer Voltage Regulation

Because a real transformer has series impedance within it, the output voltage of a transformer varies with the load even if the input voltage remains constant. The voltage regulation of a transformer is the change in the magnitude of the secondary terminal voltage from no-load to full-load.

$$\% \text{Voltage Regulation} = \frac{V_s[\text{no-load}] - V_s[\text{full-load}]}{V_s[\text{full-load}]} \times 100$$


$$\approx \frac{V_p[\text{no-load}] - V_p[\text{full-load}]}{V_p[\text{full-load}]} \times 100$$

Referred to the primary side

# SINGLE PHASE TRANSFORMER

## Voltage Regulation


Lagging Load

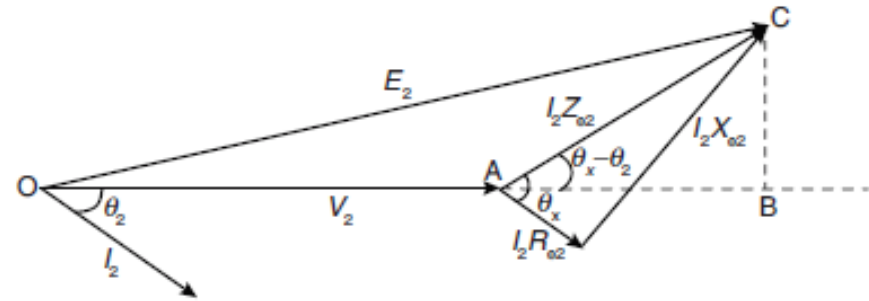

$$\text{Voltage regulation} = \frac{I_2 R_{e2} \cos \theta_2 \mp I_2 X_{e2} \sin \theta_2}{V_2} \times 100$$

Where,

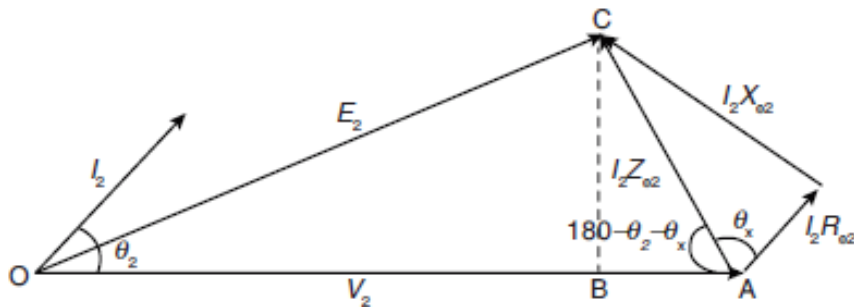– ve sign is for leading power factor and +ve sign is for lagging power factor load.



Leading Load

# SINGLE PHASE TRANSFORMER

## Determining the Values of Components in the Transformer Model

It is possible to experimentally determine the parameters of the approximate the equivalent circuit. An adequate approximation of these values can be obtained with only two tests....

- *open-circuit test*
- *short-circuit test*

