



RAMA  
UNIVERSITY

[www.ramauniversity.ac.in](http://www.ramauniversity.ac.in)

FACULTY OF ENGINEERING & TECHNOLOGY


Electrical Machine-1

Amit Kumar Singh

# THREE PHASE TRANSFORMER
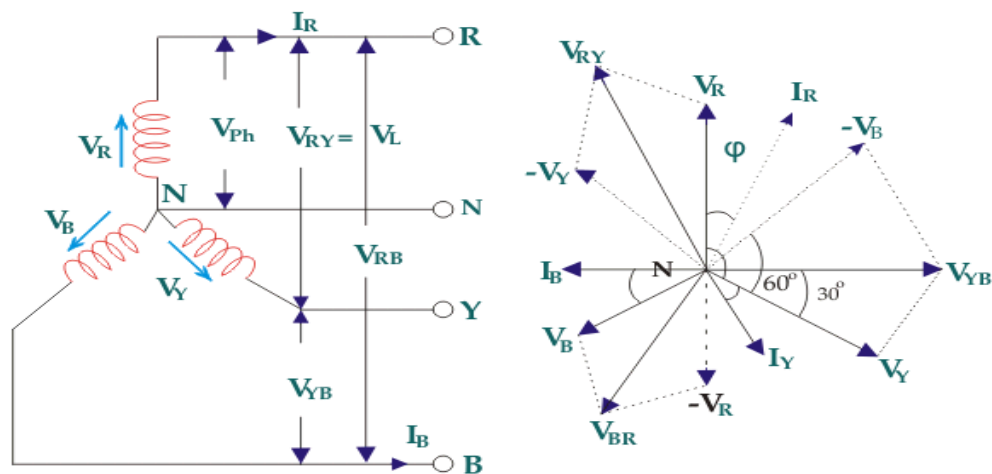
## Relationship of Line and Phase Voltages and Currents in a Star Connected System

Relationship of Line and Phase Voltages and Currents in a Star Connected System



Suppose due to load impedance the current lags the applied voltage in each phase of the system by an angle  $\phi$ . As we have considered that the system is perfectly balanced, the magnitude of current and voltage of each phase is the same. Let us say, the magnitude of the voltage across the red phase i.e. magnitude of the voltage between neutral point (N) and red phase terminal (R) is  $V_R$ .

Similarly, the magnitude of the voltage across yellow phase is  $V_Y$  and the magnitude of the voltage across blue phase is  $V_B$ . star system, magnitude of phase voltage in each phase is  $V_{ph}$ .

$$V_R = V_Y = V_B = V_{ph}$$

# THREE PHASE TRANSFORMER

We know in the star connection, line current is same as phase current. The magnitude of this current is same in all three phases and say it is  $I_L$ .

$\therefore I_R = I_Y = I_B = I_L$ , Where,  $I_R$  is line current of R phase,  $I_Y$  is line current of Y phase and  $I_B$  is line current of B phase.

Again, phase current,  $I_{ph}$  of each phase is same as line current  $I_L$  in star connected system.

$\therefore I_R = I_Y = I_B = I_L = I_{ph}$ .

Now, let us say, the voltage across R and Y terminal of the star connected circuit is  $V_{RY}$ .

The voltage across Y and B terminal of the star connected circuit is  $V_{YBB}$ .

From the diagram, it is found that


$$V_{RY} = V_R + (-V_Y)$$

$$\text{Similarly, } V_{YB} = V_Y + (-V_B)$$

$$\text{And, } V_{BR} = V_B + (-V_R)$$

Now, as angle between  $V_R$  and  $V_Y$  is  $120^\circ$ (electrical), the angle between  $V_R$  and  $-V_Y$  is  $180^\circ - 120^\circ = 60^\circ$ (electrical).

$$\begin{aligned} V_L &= |V_{RY}| = \sqrt{V_R^2 + V_Y^2 + 2V_R V_Y \cos 60^\circ} \\ &= \sqrt{V_{ph}^2 + V_{ph}^2 + 2V_{ph} V_{ph} \times \frac{1}{2}} \\ &= \sqrt{3}V_{ph} \\ \therefore V_L &= \sqrt{3}V_{ph} \end{aligned}$$

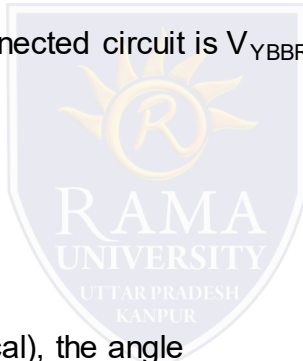

# THREE PHASE TRANSFORMER

Thus, for the star-connected system line voltage =  $\sqrt{3} \times$  phase voltage.

Line current = Phase current

As, the angle between voltage and current per phase is  $\phi$ , the electric power per phase is

$$V_{ph} I_{ph} \cos \phi = \frac{V_L}{\sqrt{3}} I_L \cos \phi$$

So the total power of three phase system is

$$3 \times \frac{V_L}{\sqrt{3}} I_L \cos \phi = \sqrt{3} V_L I_L \cos \phi$$

